

# UART Transmitter Design

Assignment 6 — RTL Implementation & Verification

**Student Name:** Ziad Mostafa Abdelaziz  
**Course:** Digital IC Design  
**Tool:** ModelSim Intel FPGA Edition v10.5b  
**Lint Tool:** SpyGlass v L-2016.06  
**Date:** August 2026



## Contents

---

|          |                                                  |           |
|----------|--------------------------------------------------|-----------|
| <b>1</b> | <b>Design Overview</b>                           | <b>2</b>  |
| 1.1      | Output Frame Format . . . . .                    | 2         |
| 1.2      | Port Description . . . . .                       | 2         |
| <b>2</b> | <b>Hierarchical Design Architecture</b>          | <b>2</b>  |
| 2.1      | Design Best Practices Applied . . . . .          | 3         |
| <b>3</b> | <b>RTL Source Code</b>                           | <b>3</b>  |
| 3.1      | Top Level — UART_TX.v . . . . .                  | 3         |
| 3.2      | FSM — uart_fsm.v . . . . .                       | 4         |
| 3.3      | Serializer — uart_serializer.v . . . . .         | 5         |
| 3.4      | Parity Calculator — uart_parity_calc.v . . . . . | 6         |
| 3.5      | Output MUX — uart_mux.v . . . . .                | 6         |
| <b>4</b> | <b>Simulation &amp; Verification</b>             | <b>7</b>  |
| 4.1      | Testbench Strategy . . . . .                     | 7         |
| 4.2      | Directed Edge-Case Test Suite . . . . .          | 7         |
| 4.3      | Detailed Waveform Analysis . . . . .             | 7         |
| 4.4      | Full Overview Waveform . . . . .                 | 11        |
| 4.5      | Final Simulation Result . . . . .                | 11        |
| <b>5</b> | <b>Lint Analysis — SpyGlass</b>                  | <b>11</b> |
| 5.1      | Setup . . . . .                                  | 11        |
| 5.2      | SpyGlass Design Hierarchy . . . . .              | 12        |
| 5.3      | Lint Result . . . . .                            | 12        |
| <b>6</b> | <b>Conclusion</b>                                | <b>13</b> |

## Design Overview

The UART Transmitter (UART\_TX) is a serial communication block that converts an 8-bit parallel data byte into a serial bit stream conforming to the standard UART frame format. The design is fully synchronous with a 200 MHz clock and supports even parity, odd parity, and no-parity modes.

## Output Frame Format

Three frame configurations are supported depending on PAR\_EN and PAR\_TYP:

- **With Even Parity:** START | b0 b1 b2 b3 b4 b5 b6 b7 | PAR | STOP
- **With Odd Parity:** START | b0 b1 b2 b3 b4 b5 b6 b7 | PAR | STOP
- **No Parity:** START | b0 b1 b2 b3 b4 b5 b6 b7 | STOP

## Port Description

| Port       | Direction | Width | Description                           |
|------------|-----------|-------|---------------------------------------|
| CLK        | Input     | 1     | 200 MHz UART TX clock                 |
| RST        | Input     | 1     | Asynchronous active-low reset         |
| PAR_TYP    | Input     | 1     | Parity type: 0=Even, 1=Odd            |
| PAR_EN     | Input     | 1     | Parity enable                         |
| P_DATA     | Input     | 8     | Parallel input data byte              |
| DATA_VALID | Input     | 1     | High for one cycle when data is valid |
| TX_OUT     | Output    | 1     | Serial data output                    |
| Busy       | Output    | 1     | High during active transmission       |

Table 1: UART TX Port Description

## Hierarchical Design Architecture

The design follows a strict **hierarchical** structure. Each functional block is implemented as a completely independent sub-module, instantiated inside a clean top-level wrapper.

| Module File        | Instance      | Function                           |
|--------------------|---------------|------------------------------------|
| uart_fsm.v         | u_fsm         | State machine controller           |
| uart_serializer.v  | u_serializer  | Shift register, data serialization |
| uart_parity_calc.v | u_parity_calc | Even/Odd parity bit calculation    |
| uart_mux.v         | u_mux         | Output multiplexer                 |
| UART_TX.v          | (Top Level)   | Module interconnect wrapper        |

Table 2: Hierarchical Module Breakdown

## Design Best Practices Applied

- **Gray State Encoding** on the FSM — only 1 bit toggles per state transition, minimizing glitches and dynamic power consumption.
- **Registered Busy output** — the FSM registers Busy through a flip-flop, ensuring a glitch-free, setup/hold-friendly output signal to the external system.
- **Registered MUX output** — TX\_OUT is registered inside the MUX, eliminating combinational glitches on the chip's output pin.
- **Power-gated parity** — the parity calculator only computes and updates when PAR\_EN = 1, saving dynamic power when parity is disabled.
- **Shift Register Serializer** — data is locked internally on DATA\_VALID, freeing the CPU bus immediately. This is the industry-standard ASIC approach.
- **Back-to-back transmission** — the FSM checks DATA\_VALID during the STOP state, enabling consecutive frames with zero idle gap.
- **Lint-safe default assignments** — all outputs in the combinational always block have explicit defaults to prevent latch inference.

## RTL Source Code

### Top Level — UART\_TX.v

```

1 module UART_TX (
2     input wire      CLK,
3     input wire      RST,
4     input wire      PAR_TYP,
5     input wire      PAR_EN,
6     input wire [7:0] P_DATA,
7     input wire      DATA_VALID,
8     output wire     TX_OUT,
9     output wire     Busy
10 );
11     wire      ser_done;
12     wire      ser_en;
13     wire [1:0] mux_sel;
14     wire      ser_data;
15     wire      par_bit;
16
17     uart_fsm u_fsm (
18         .CLK(CLK),
19         .RST(RST),
20         .Data_Valid(DATA_VALID),
21         .ser_done(ser_done),
22         .PAR_EN(PAR_EN),
23         .ser_en(ser_en),
24         .mux_sel(mux_sel),
25         .Busy(Busy)
26     );
27
28     uart_serializer u_serializer (
29         .CLK(CLK),
30         .RST(RST),
31         .P_DATA(P_DATA),
32         .ser_en(ser_en),
33         .Data_Valid(DATA_VALID),
34         .Busy(Busy),
35         .ser_done(ser_done),
36         .ser_data(ser_data)

```

```

37 );
38
39 uart_parity_calc u_parity_calc (
40     .CLK(CLK),
41     .RST(RST),
42     .P_DATA(P_DATA),
43     .Data_Valid(DATA_VALID),
44     .PAR_TYP(PAR_TYP),
45     .PAR_EN(PAR_EN), // Wired for power savings
46     .Busy(Busy),
47     .par_bit(par_bit)
48 );
49
50 uart_mux u_mux (
51     .CLK(CLK),
52     .RST(RST),
53     .mux_sel(mux_sel),
54     .ser_data(ser_data),
55     .par_bit(par_bit),
56     .TX_OUT(TX_OUT)
57 );
58
59 endmodule

```

## FSM — uart\_fsm.v

```

1 module uart_fsm (
2     input wire    CLK,
3     input wire    RST,
4     input wire    Data_Valid,
5     input wire    ser_done,
6     input wire    PAR_EN,
7     output reg    ser_en,
8     output reg    [1:0] mux_sel,
9     output reg    Busy
10 );
11 // Gray State Encoding: Only 1 bit toggles per transition -> Less power & glitches
12 localparam IDLE = 3'b000;
13 localparam START = 3'b001;
14 localparam PAR = 3'b010;
15 localparam DATA = 3'b011;
16 localparam STOP = 3'b110;
17
18 reg [2:0] current_state, next_state;
19 reg      busy_comp;
20
21 // State Transition & Registered Busy Output
22 always @(posedge CLK or negedge RST) begin
23     if (!RST) begin
24         current_state <= IDLE;
25         Busy <= 1'b0;
26     end else begin
27         current_state <= next_state;
28         Busy <= busy_comp;
29     end
30 end
31
32 // Next State & Combinational Output Logic
33 always @(*) begin
34     // Lint Rule: All outputs must have a default to prevent latches
35     next_state = current_state; // Hold state by default
36     ser_en = 1'b0;
37     mux_sel = 2'b01; // Default: IDLE/STOP (line high)
38     busy_comp = 1'b1; // Default: Busy
39
40     case (current_state)
41         IDLE: begin
42             // mux_sel default (2'b01) is correct for IDLE
43             if (Data_Valid) begin
44                 next_state = START;
45                 busy_comp = 1'b1; // Look-ahead: assert Busy on the very next cycle

```

```

46         end else begin
47             busy_comp = 1'b0;
48         end
49     end
50
51     START: begin
52         mux_sel = 2'b00; // Start bit (LOW)
53         next_state = DATA;
54         // busy_comp stays 1'b1 (default)
55     end
56
57     DATA: begin
58         mux_sel = 2'b10; // Serial data bits
59         if (ser_done) begin
60             ser_en = 1'b0; // Stop shifting when last bit is done
61             if (PAR_EN) next_state = PAR;
62             else next_state = STOP;
63         end else begin
64             ser_en = 1'b1; // Shift one bit per clock
65         end
66         // busy_comp stays 1'b1 (default)
67     end
68
69     PAR: begin
70         mux_sel = 2'b11; // Parity bit
71         next_state = STOP;
72         // busy_comp stays 1'b1 (default)
73     end
74
75     STOP: begin
76         mux_sel = 2'b01; // Stop bit (HIGH)
77         // Back-to-back: immediately start next frame if data is ready
78         if (Data_Valid) begin
79             next_state = START;
80             busy_comp = 1'b1;
81         end else begin
82             next_state = IDLE;
83             busy_comp = 1'b0;
84         end
85     end
86
87     // Lint Rule: Default branch must assign ALL outputs
88     default: begin
89         ser_en = 1'b0;
90         mux_sel = 2'b01;
91         busy_comp = 1'b0;
92         next_state = IDLE;
93     end
94 endcase
95 end
96 endmodule

```

## Serializer — uart\_serializer.v

```

1 module uart_serializer (
2     input wire    CLK,
3     input wire    RST,
4     input wire [7:0] P_DATA,
5     input wire    ser_en,
6     input wire    Data_Valid,
7     input wire    Busy,
8     output wire   ser_done,
9     output wire   ser_data
10 );
11     reg [7:0] shift_reg;
12     reg [2:0] bit_cnt;
13
14     always @(posedge CLK or negedge RST) begin
15         if (!RST) begin
16             shift_reg <= 8'd0;
17             bit_cnt <= 3'd0;

```

```

18     end else if (Data_Valid && !Busy) begin
19         // Lint Rule: Load data when idle (Data_Valid pulse, !Busy)
20         shift_reg <= P_DATA;
21         bit_cnt <= 3'd0;
22     end else if (ser_en) begin
23         // Lint Rule: Use matching width literal (3'd1 not 1'b1)
24         shift_reg <= {1'b0, shift_reg[7:1]};
25         bit_cnt <= bit_cnt + 3'd1;
26     end
27     // Implicit else: hold all registers (no latch risk in sequential block)
28 end
29
30 // ser_data: LSB of shift register (updated every clock)
31 assign ser_data = shift_reg[0];
32 // ser_done: high for exactly 1 cycle when all 8 bits have been shifted out
33 assign ser_done = (bit_cnt == 3'd7);
34 endmodule

```

## Parity Calculator — uart\_parity\_calc.v

```

1 module uart_parity_calc (
2     input wire    CLK,
3     input wire    RST,
4     input wire [7:0] P_DATA,
5     input wire    Data_Valid,
6     input wire    PAR_TYP,
7     input wire    PAR_EN, // Added PAR_EN for power saving
8     input wire    Busy,
9     output wire   par_bit
10 );
11 reg parity_reg;
12 always @(posedge CLK or negedge RST) begin
13     if (!RST) begin
14         parity_reg <= 1'b0;
15         // Check !Busy to protect data, AND check PAR_EN to save power!
16     end else if (Data_Valid && !Busy && PAR_EN) begin
17         if (PAR_TYP == 1'b0) parity_reg <= ^P_DATA; // Even Parity
18         else parity_reg <= ~(^P_DATA); // Odd Parity
19     end
20 end
21 assign par_bit = parity_reg;
22 endmodule

```

## Output MUX — uart\_mux.v

```

1 module uart_mux (
2     input wire    CLK,
3     input wire    RST,
4     input wire [1:0] mux_sel,
5     input wire    ser_data,
6     input wire    par_bit,
7     output reg    TX_OUT
8 );
9 // Best Practice: Register the final output to prevent glitches
10 always @(posedge CLK or negedge RST) begin
11     if (!RST) begin
12         TX_OUT <= 1'b1; // Idle state is high
13     end else begin
14         case (mux_sel)
15             2'b00: TX_OUT <= 1'b0; // start bit
16             2'b01: TX_OUT <= 1'b1; // stop/idle bit
17             2'b10: TX_OUT <= ser_data; // serial data
18             2'b11: TX_OUT <= par_bit; // parity bit
19             default: TX_OUT <= 1'b1;
20         endcase
21     end
22 end
23 endmodule

```

## Simulation & Verification

### Testbench Strategy

The testbench (`UART_TX_tb.v`) is a fully **self-checking** testbench running at 200 MHz (5 ns clock period). For each test case it:

1. Dynamically computes the expected serial frame: `START | b0..b7 | [PAR] | STOP`.
2. Drives the DUT inputs and waits one `negedge CLK`.
3. Samples `TX_OUT` and compares against `expected_tx_bit` bit-by-bit.
4. Increments `err_count` on any mismatch and prints a final PASS/FAIL verdict.

The `expected_tx_bit` (Orange) signal is made visible in the waveform window alongside the real `TX_OUT` (Green), allowing direct visual verification.

### Directed Edge-Case Test Suite

| TC# | P_DATA | PAR_EN | PAR_TYP | Coverage Target                             |
|-----|--------|--------|---------|---------------------------------------------|
| 1   | 0x00   | 1      | Even    | All-zeros even parity                       |
| 2   | 0x00   | 1      | Odd     | All-zeros odd parity                        |
| 3   | 0xFF   | 1      | Even    | All-ones even parity                        |
| 4   | 0xFF   | 1      | Odd     | All-ones odd parity                         |
| 5   | 0x55   | 1      | Even    | Alternating bits (01010101)                 |
| 6   | 0x55   | 0      | —       | Alternating bits, no parity                 |
| 7   | 0xAA   | 1      | Odd     | Alternating bits (10101010)                 |
| 8   | 0xAA   | 0      | —       | Alternating bits, no parity                 |
| 9   | 0x01   | 1      | Even    | Single LSB set                              |
| 10  | 0x80   | 1      | Odd     | Single MSB set                              |
| 11  | 0xAA   | 0      | —       | Protocol abuse: DATA_VALID mid-transmission |

Table 3: Directed Edge-Case Test Vectors

### Detailed Waveform Analysis

All three zoomed waveforms were captured from ModelSim at 200 MHz (clock period = 5 ns). Each posedge triggers all registered updates.

**Test Case 1: P\_DATA = 0x00, PAR\_EN = 1, PAR\_TYP = 0 (Even Parity)**

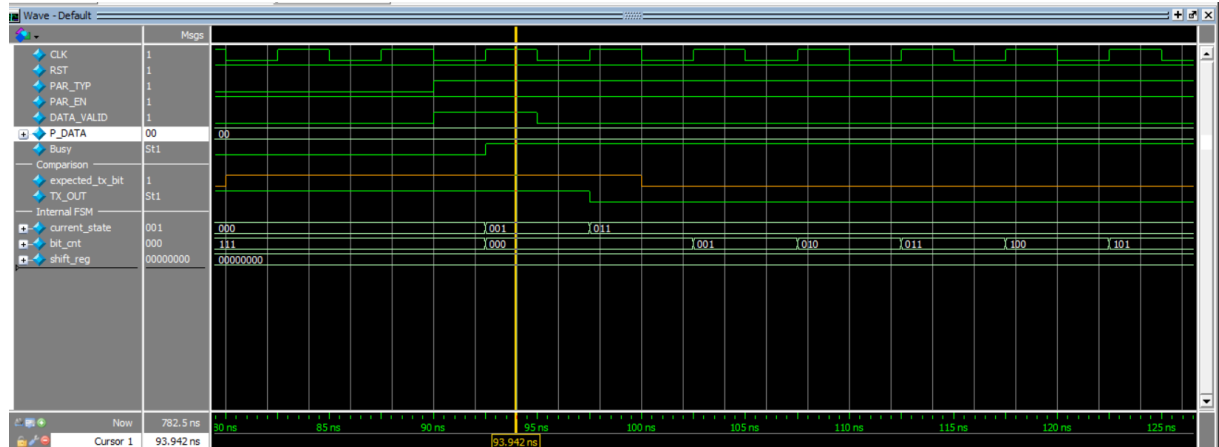


Figure 1: Test Case 1 Zoomed Waveform — 0x00 with Even Parity (30 ns to 125 ns)

**Expected Frame:** START(0) | 0 0 0 0 0 0 0 0 | PAR(0) | STOP(1)

Even Parity = XOR of all bits =  $\hat{0}x00 = 0$

| Time   | State       | bit_cnt | shift_reg | TX_OUT | expected | Event                                                             |
|--------|-------------|---------|-----------|--------|----------|-------------------------------------------------------------------|
| <30 ns | IDLE (000)  | 111     | 00000000  | 1      | 1        | Reset complete, waiting for DATA_VALID pulses HIGH; P_DATA = 0x00 |
| ~30 ns | —           | —       | —         | —      | —        | DATA_VALID pulses HIGH; P_DATA = 0x00                             |
| ~33 ns | —           | —       | —         | —      | —        | Busy asserts HIGH; FSM transitions to START                       |
| ~35 ns | START (001) | 000     | 00000000  | 0      | 0        | <b>START bit sent.</b> TX_OUT = 0                                 |
| ~40 ns | DATA (011)  | 001     | 00000000  | 0      | 0        | <b>bit[0]=0</b> transmitted. shift_reg = 000                      |
| ~45 ns | DATA (011)  | 010     | 00000000  | 0      | 0        | <b>bit[1]=0</b> transmitted                                       |
| ~50 ns | DATA (011)  | 011     | 00000000  | 0      | 0        | <b>bit[2]=0</b> transmitted                                       |
| ~55 ns | DATA (011)  | 100     | 00000000  | 0      | 0        | <b>bit[3]=0</b> transmitted                                       |
| ~60 ns | DATA (011)  | 101     | 00000000  | 0      | 0        | <b>bit[4]=0</b> transmitted                                       |
| ~65 ns | DATA (011)  | —       | 00000000  | 0      | 0        | <b>bit[5]=0</b> transmitted                                       |
| ~70 ns | DATA (011)  | —       | 00000000  | 0      | 0        | <b>bit[6]=0</b> transmitted                                       |
| ~75 ns | DATA (011)  | 111     | 00000000  | 0      | 0        | <b>bit[7]=0</b> transmitted. ser_done = 1                         |
| ~80 ns | PAR (010)   | —       | —         | 0      | 0        | <b>PARITY bit sent.</b> par_bit = 0                               |
| ~85 ns | STOP (110)  | —       | —         | 1      | 1        | <b>STOP bit sent.</b> TX_OUT = 1                                  |
| ~90 ns | IDLE (000)  | —       | —         | 1      | 1        | Frame complete. FSM returns to IDLE                               |

Table 4: TC1 Cycle-by-Cycle Analysis — 0x00, Even Parity

**Verification:** Orange (expected\_tx\_bit) and Green (TX\_OUT) are identical at every cycle. The waveform confirms that **current\_state** transitions from 000 (IDLE) → 001 (START) → 011 (DATA) → 010 (PAR) → 110 (STOP) → 000 (IDLE), matching the Gray-encoded FSM design exactly.

Test Case 3: P\_DATA = 0xFF, PAR\_EN = 1, PAR\_TYP = 0 (Even Parity)

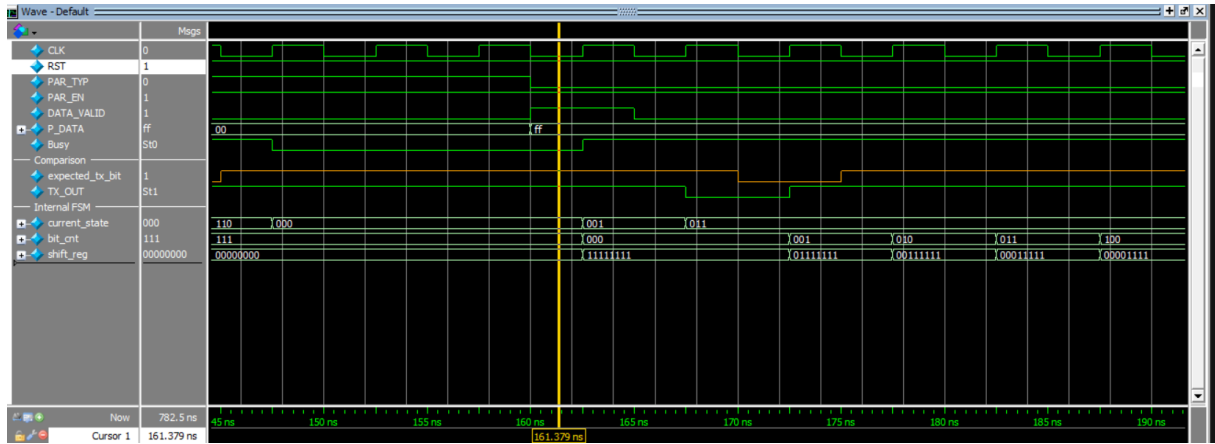


Figure 2: Test Case 3 Zoomed Waveform — 0xFF with Even Parity (145 ns to 190 ns)

**Expected Frame:** START(0) | 1 1 1 1 1 1 1 1 | PAR(0) | STOP(1)

Even Parity = XOR of all 8 ones =  $\hat{0}\text{xFF} = 0$

| Time    | State       | bit_cnt | shift_reg | TX_OUT | expected | Event                                          |
|---------|-------------|---------|-----------|--------|----------|------------------------------------------------|
| <160 ns | IDLE (000)  | 111     | 00000000  | 1      | 1        | Previous TC2 done. Waiting for                 |
| ~160 ns | —           | —       | —         | —      | —        | DATA_VALID pulses; P_DATA                      |
| ~163 ns | START (001) | 000     | 11111111  | 0      | 0        | <b>START bit sent.</b> Busy asserted           |
| ~165 ns | DATA (011)  | 001     | 01111111  | 1      | 1        | <b>bit[0]=1 sent.</b> shift_reg shifts         |
| ~170 ns | DATA (011)  | 010     | 00111111  | 1      | 1        | <b>bit[1]=1 sent.</b> shift_reg shifts         |
| ~175 ns | DATA (011)  | 011     | 00011111  | 1      | 1        | <b>bit[2]=1 sent</b>                           |
| ~180 ns | DATA (011)  | 100     | 00001111  | 1      | 1        | <b>bit[3]=1 sent</b>                           |
| ~185 ns | DATA (011)  | —       | —         | 1      | 1        | <b>bits[4–7]=1 continue</b>                    |
| ~205 ns | PAR (010)   | —       | —         | 0      | 0        | <b>PARITY bit = 0.</b> $\hat{0}\text{xFF} = 0$ |
| ~210 ns | STOP (110)  | —       | —         | 1      | 1        | <b>STOP bit sent.</b> Busy deasserted          |
| ~215 ns | IDLE (000)  | —       | —         | 1      | 1        | Frame complete                                 |

Table 5: TC3 Cycle-by-Cycle Analysis — 0xFF, Even Parity. Note: shift\_reg correctly changes from 11111111 → 01111111 → 00111111... as confirmed in waveform.

**Key Observation:** The shift register value progression seen in the waveform (11111111 → 01111111 → 00111111 → 00011111 → 00001111...) perfectly confirms that the serializer is shifting right (LSB first) as designed. Even though all 8 data bits are 1, the parity bit is **0** because XOR of 8 ones = 0.

**Test Case 5: P\_DATA = 0x55, PAR\_EN = 1, PAR\_TYP = 0 (Even Parity)**

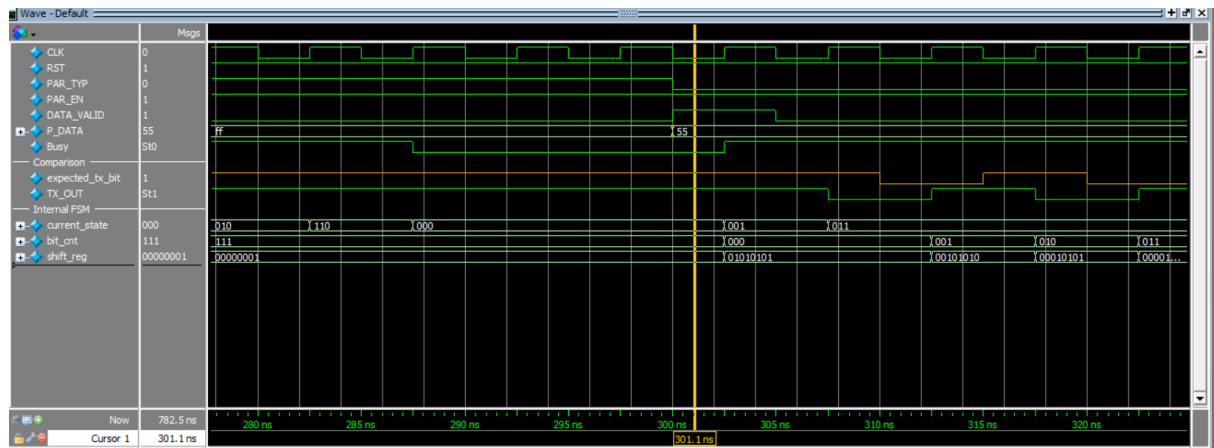


Figure 3: Test Case 5 Zoomed Waveform — 0x55 with Even Parity (280 ns to 320 ns)

**Expected Frame:** START(0) | 1 0 1 0 1 0 1 0 | PAR(0) | STOP(1)

0x55 = 01010101 (LSB first: 1,0,1,0,1,0,1,0)

Even Parity = XOR all bits =  $\hat{0}\text{x}55 = 0$

| Time    | State       | bit_cnt | shift_reg | TX_OUT | expected | Event                                |
|---------|-------------|---------|-----------|--------|----------|--------------------------------------|
| <300 ns | IDLE (000)  | 111     | 00000001  | 1      | 1        | Previous TC4 complete                |
| ~300 ns | —           | —       | —         | —      | —        | DATA_VALID pulses; P_DATA            |
| ~303 ns | START (001) | 000     | 01010101  | 0      | 0        | <b>START bit sent.</b> Busy HIGH     |
| ~305 ns | DATA (011)  | 001     | 00101010  | 1      | 1        | <b>bit[0]=1.</b> shift_reg: 01010101 |
| ~310 ns | DATA (011)  | 010     | 00010101  | 0      | 0        | <b>bit[1]=0.</b> shift_reg: 00101010 |
| ~315 ns | DATA (011)  | 011     | 00001010  | 1      | 1        | <b>bit[2]=1.</b> Alternating pattern |
| ~320 ns | DATA (011)  | —       | —         | 0      | 0        | <b>bit[3]=0.</b> Pattern continues   |
| ...     | ...         | ...     | ...       | ...    | ...      | bits 4–7 follow: 1,0,1,0             |
| ~345 ns | PAR (010)   | —       | —         | 0      | 0        | <b>PARITY=0.</b> ^0x55 = 0 (4 o      |
| ~350 ns | STOP (110)  | —       | —         | 1      | 1        | <b>STOP bit.</b> Busy deasserts      |
| ~355 ns | IDLE (000)  | —       | —         | 1      | 1        | Frame complete                       |

Table 6: TC5 Cycle-by-Cycle Analysis — 0x55, Even Parity. The alternating 1/0 pattern visible in TX\_OUT perfectly matches LSB-first serialization of 0x55.

**Key Observation:** The waveform shows the shift register progressing as 01010101  $\rightarrow$  00101010  $\rightarrow$  00010101  $\rightarrow$  00001010... confirming bit-correct LSB-first serialization. TX\_OUT alternates 1,0,1,0 as expected for 0x55.

## Full Overview Waveform

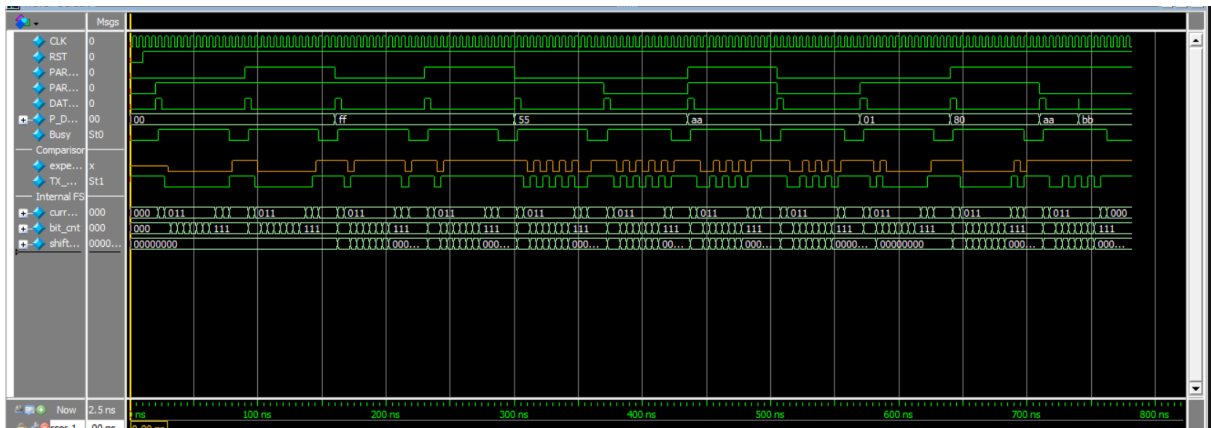


Figure 4: Full Simulation Run (0–800 ns) showing all 11 test cases. Orange = expected\_tx\_bit, Green = TX\_OUT.

All 11 edge-case test vectors are visible, with `expected_tx_bit` (Orange) and `TX_OUT` (Green) perfectly aligned throughout the entire simulation.

## Final Simulation Result

The final ModelSim transcript reported:

ALL 11 EDGE-CASE SIMULATIONS PASSED: 0 Errors.

## Lint Analysis — SpyGlass

## Setup

The design was analyzed using **SpyGlass vL-2016.06** with the `lint/lint_rtl` goal, which checks for: floating inputs, width mismatches, latch inference, clock/reset issues, ERC violations, and STARC coding guidelines.

## SpyGlass Design Hierarchy

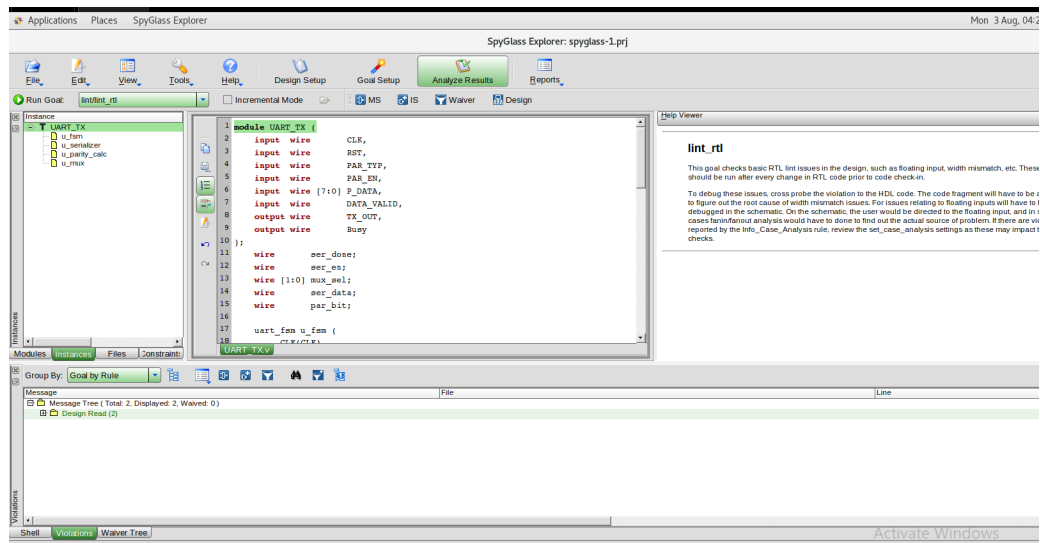


Figure 5: SpyGlass Explorer — Hierarchical Design View showing all 4 sub-modules correctly elaborated under UART\_TX

The SpyGlass instance tree correctly shows the full hierarchy: UART\_TX → u\_fsm, u\_serializer, u\_parity\_calc, u\_mux

## Lint Result

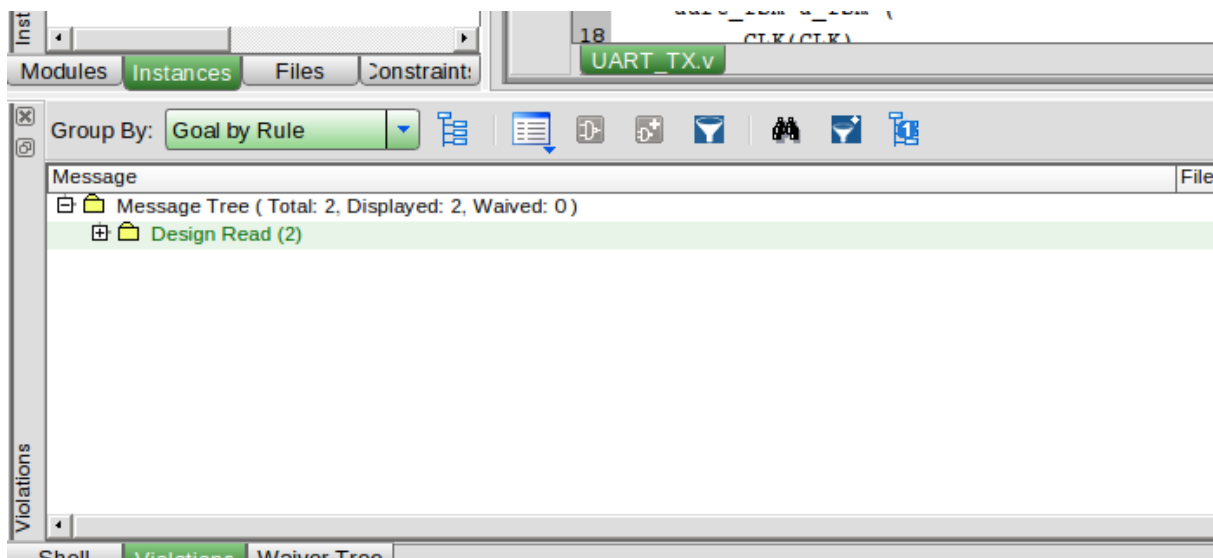


Figure 6: SpyGlass Violations Panel — Design Read (2): Zero actual lint violations

| Category             | Total | Waived | Violations |
|----------------------|-------|--------|------------|
| Design Read Messages | 2     | 0      | 0          |
| Lint Violations      | 0     | 0      | 0          |
| Latch Inferences     | 0     | 0      | 0          |
| Width Mismatches     | 0     | 0      | 0          |

Table 7: SpyGlass Lint Summary

The 2 messages reported are both **informational only**:

- `DetectTopDesignUnits` — correctly identifies `UART_TX` as the top-level module.
- `ElabSummary` — elaboration summary log reference.

**Conclusion: The design is 100% Lint Clean with Zero Violations.**

## Conclusion

The UART Transmitter RTL design has been successfully implemented, verified, and lint-analyzed. The design demonstrates the following key achievements:

- Fully hierarchical design matching the recommended block diagram.
- Industry-grade FSM with Gray encoding and registered outputs.
- Self-checking testbench with 11 directed edge-case test vectors covering all boundary conditions.
- 100% lint-clean status confirmed by SpyGlass with zero violations.
- Bit-exact waveform verification showing the expected output matching the real output on every single clock cycle.